

1E1006

Roll No. _____

[Total No. of Pages : 4]

1E1006

B.Tech. I - Sem.(Reback) Exam - Jan-Feb. 2012

105(O) - Electrical & Electronics Engg.

(Common to all Branches of Engg.)

Time : 3 Hours

Maximum Marks : 80

Min. Passing Marks : 24

Instructions to Candidates:

Attempt overall **five questions** selecting **one question** from each unit. All questions carry **equal marks**. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.


Use of following supporting material is permitted during examination. (Mentioned in form No. 205)

1. Nil 2. Nil

Unit - I

1. (a) What are the Kirchoff's laws. Explain how does the application of Kirchoff's Laws help in getting the solution of D.C. Circuits. 6
1. (b) Three resistances $R_1=100\Omega$, $R_2=60\Omega$, $R_3=40$ are connected in delta between the terminal points CDE, as shown in figure 1 to the source of 160 Volts supply AB through two resistances $R_4=88$ and $R_5=80$. Determine the currents flowing through ckt between A and B and also through R_4 and R_5 . 10

FIGURE 1

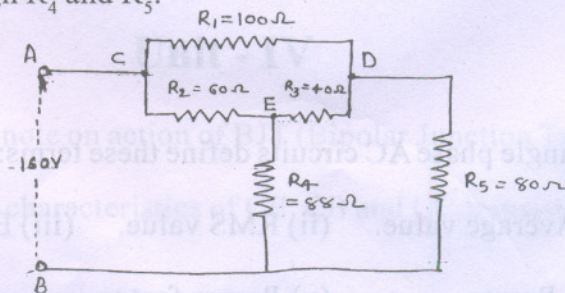

1E1006



1E1006


1

[Contd...]

OR

- 1 (a) State and Explain Thevenin's theorem. Using it find current through the galvanometer of Wheat Stone bridge given in figure 2. 10

FIGURE 2

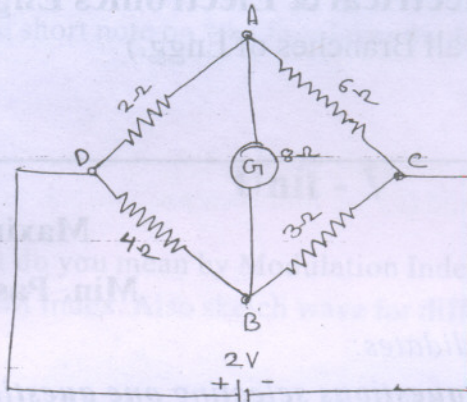


- (b) State and Explain Superposition theorem. 6

Unit - II

2. (a) For the series parallel circuit shown in figure 3 determine (a) the total impedance between the terminals a, b and state if it is inductive or capacitive (b) the voltage across in the parallel branch, and (c) the phase angle. 6

FIGURE 3

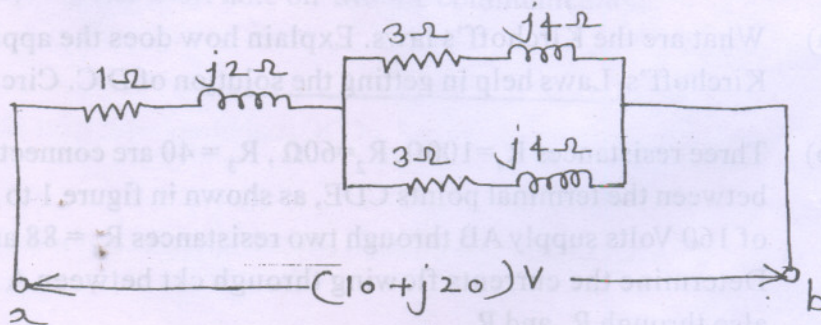

- (b) In single phase AC circuits define these terms:

- (i) Average value. (ii) RMS value. (iii) Effective value.
(iv) Power. (v) Power factor. 5

1E1006



1E1006

2


[Contd...]

- (c) Find the total current to the parallel circuit with $L=0.05H$ and $C=0.66\mu F$ with an applied. Voltage of $V=200 \sin 5000t V$. 5

OR

2. (a) Explain the process of measurement of power in h^{3-0} Balanced circuit? 8
- (b) A delta connected load is arranged as in figure 4. Calculate (a) the phase currents and (b) the line currents. The supply Voltage is 400V at 50HZ. 8

FIGURE 4

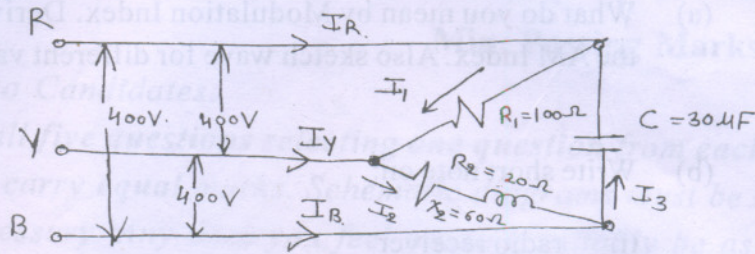

Unit - III

3. (a) Explain the Construction and Operation of single phase Transformer. 10
- (b) Obtain the E.M.F. equation of a transformer and draw the phases diagram under no load condition. 6

OR

3. (a) Describe the working principle of DC machines with neat sketch. 6
- (b) Describe in detail the construction of different parts of a DC generator. 10

Unit - IV

4. (a) Write short note on action of BJT (Bipolar Junction Transistor). 8
- (b) Discuss the characteristics of CE, CB and CC transistor Amplifiers. 8



OR

4. (a) What do you understand by negative resistance, explain the occurrence of negative resistance regions in UJT and triode. 10

(b) Write short note on "the four layer diode"? 6

Unit - V

5. (a) What do you mean by Modulation Index. Derive an expression for the AM Index. Also sketch wave for different value of index. 8

(b) Write short note on:

(i) radio receiver

(ii) television 8

OR

5. (a) Explain elementary concepts of Optical Communication? 5

(b) Define the terms modulation, demodulation in brief. 5

(c) Write short note on Mobile communication. 6

