

(b)

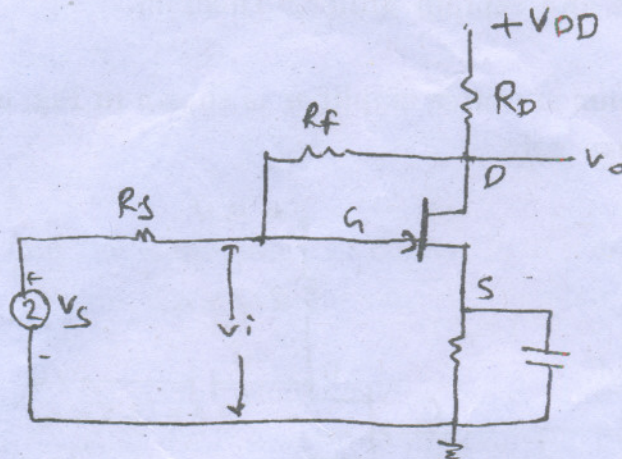


Fig. 4

Calculate the voltage gain with and without feedback for the circuit given in Fig. 4 with values,  $g_m = 5 \text{ mA/V}$ ,  $R_D = 5.1 \text{ k}\Omega$ ,  $R_s = 1 \text{ k}\Omega$ ,  $R_f = 20 \text{ k}\Omega$ ,  $r_d = 1 \text{ M}\Omega$ .

8

### UNIT - V

5 (a) Draw the circuit of an Astable multivibrator and explain its working.

8

(b) Explain the Barkhausen criterion for sustained oscillations. Draw the R-C phase shift oscillator circuit and describe its working.

8

OR

5 Write short notes on the following :

(a) Wien bridge oscillators

(b) Schmitt trigger.

16

