

UNIT - IV

- 4 (a) Explain how input resistance of an emitter follower can be increased by using darlington circuit. What is the biasing problem associated with this circuit ? 8
- (b) A multistage amplifier consists of three stages; the voltage gains of the stages are 30, 50 and 60. Calculate the overall gain in db. 4
- (c) Explain Miller's theorem. 4

OR

- 4 (a) Discuss the frequency response curve of R-C coupled amplifier by deriving suitable derivation for low and high frequency. 8
- (b) Explain bootstrapped darlington circuit. 8

UNIT - V

- 5 (a) Prove that is a negative feedback amplifier

$$\left| \frac{dA_f}{A_f} \right| = \frac{1}{|1 + \beta A|} \left| \frac{dA}{A} \right|$$

where A_f = gain with feedback

A = transfer gain

β = feedback factor

7

