

**3E1493**

Roll No. : \_\_\_\_\_

Total Printed Pages : **8****3E1493**

B. Tech. (Sem. III) (Main & Back) Examination, January - 2013  
 Electronics & Communication  
 3EC3 Circuit Analysis & Synthesis (Common for AI, EC & EI)

Time : 3 Hours]

[Total Marks : 80

[Min. Passing Marks : 24

Attempt any **five** questions. **Selecting one** question from each unit.  
 All questions carry **equal** marks. Schematic diagrams must  
 be shown wherever necessary. Any data you feel missing  
 suitably be assumed and stated clearly. Units of quantities  
 used/calculated must be stated clearly.

Use of following supporting material is permitted during examination.  
 (Mentioned in form No. 205)

1. NIL2. NIL**UNIT - I**

- 1 (a) What do you understand by the term compensation ? For a linear time-invariant network as given in **fig. 1.1**, deduce the change in the current, if the impedance of an uncoupled branch is changed. Find the voltage across BD, when the resistor in the branch BC is changed from  $R$  to  $(R + \Delta R)$ .

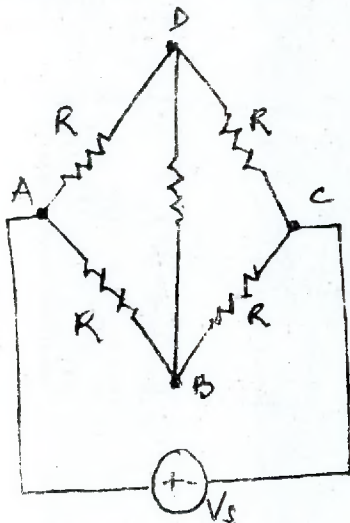


Figure 1.1

8



- (b) Calculate the effective inductance of the circuit given in fig. 1.2 across AB.

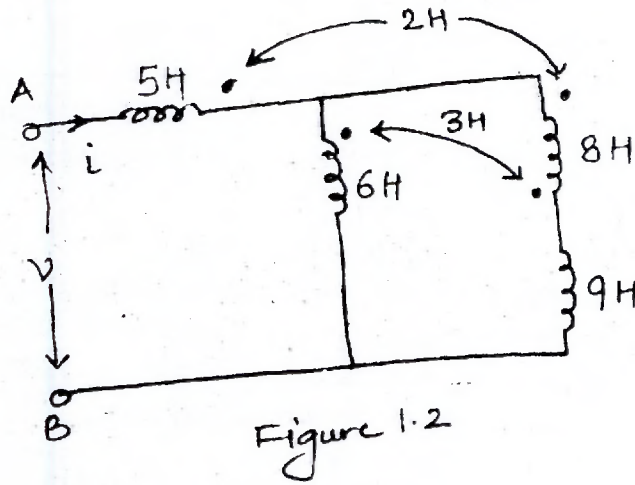


Figure 1.2

8

OR

- 1 (a) Determine the Thevenin's equivalent of the circuit shown in fig. 1.3.

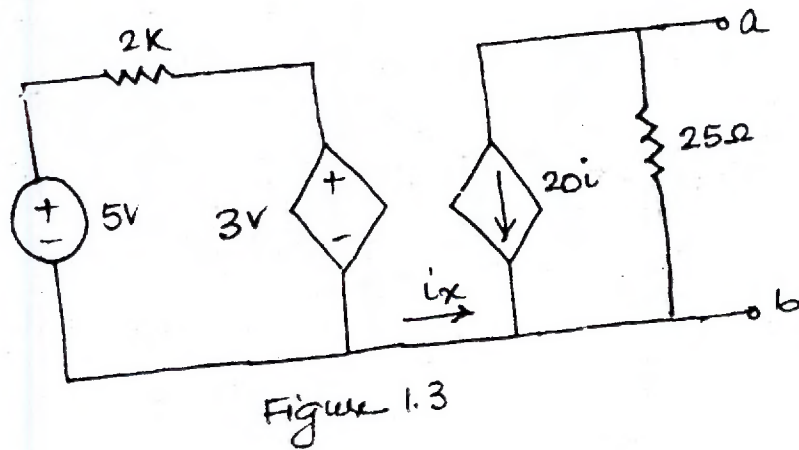


Figure 1.3

8

[Contd...]



- (b) Determine the load resistance to receive maximum power from the source. Also, find the maximum power delivered to the load in the circuit given in **fig. 1.4**.

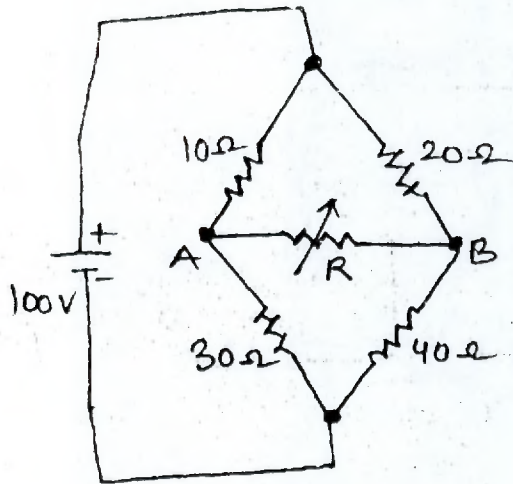


Figure 1.4

8

## UNIT - II

- 2 (a) Find out the unit step response for  $i_L$  in the network given in **fig. 2.1**, for a given condition that  $i_L(0) = 0$ .

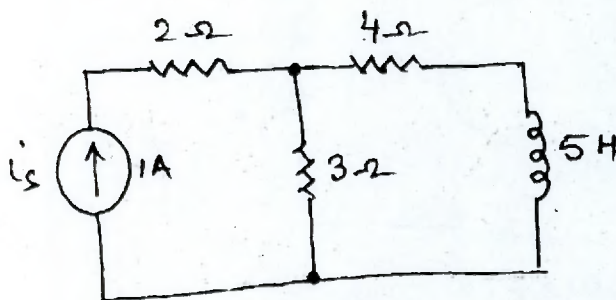


Figure 2.1

8



- (b) The circuit shown in **fig. 2.2**, consists of a series RLC circuit with  $R=10\Omega$ ,  $L=0.5H$ ,  $C=200\mu F$  has a sinusoidal voltage  $v=150\sin(200t+\phi)$ . If the switch is closed at  $\phi=30^\circ$ , determine the current equation.

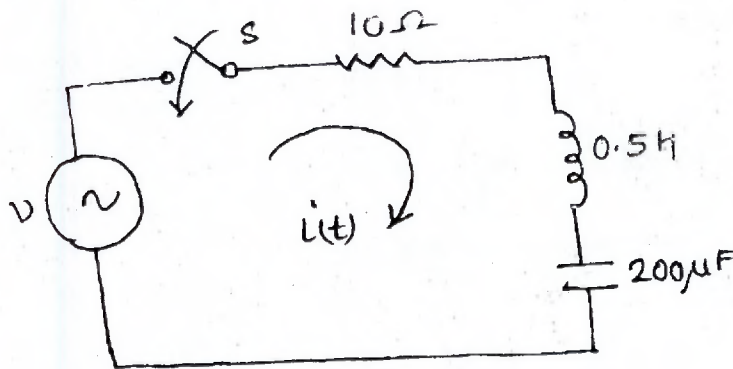


Figure 2.2

8

OR

- 2 (a) In a series RL circuit shown in **fig. 2.3**, a sinusoidal voltage  $v=V_m \sin \omega t$  is applied at  $t=0$  through the switch 'S'. The switch has been open for a long time. Use Laplace transformation method to determine  $i_L(t)$  for  $t>0$ .

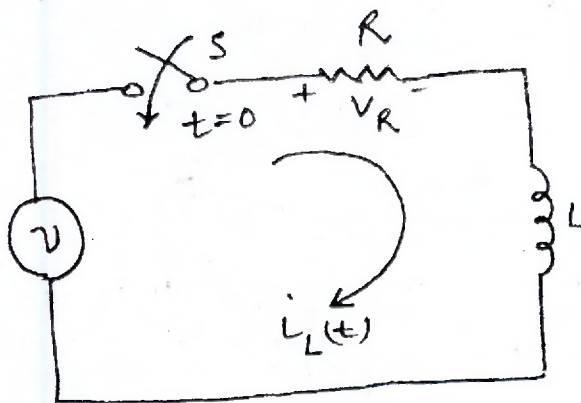


Figure 2.3

8



- (b) Determine the Fourier series expansion of the periodic waveform given in fig. 2.4.

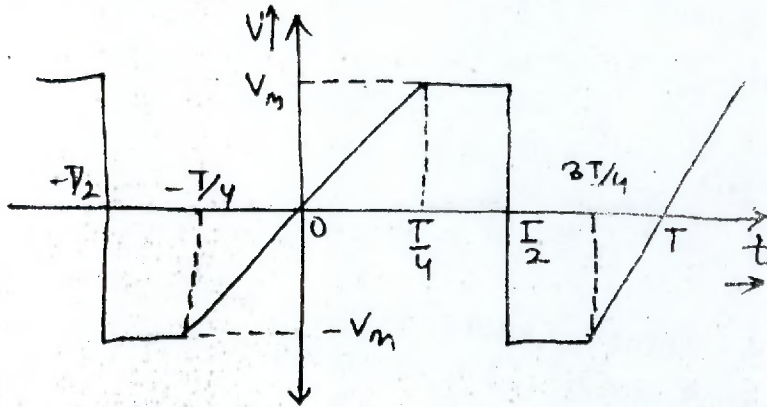


Figure 2.4

8

UNIT - III

- 3 (a) In a two-port network, the voltage gain is given by :

$$\frac{V_2(s)}{V_1(s)} = \frac{s+2}{s^2+1}$$

Determine the output voltage, if the input is :

- (i) a unit impulse
- (ii) a unit step
- (iii)  $e^{-t}$

6

- (b) For the network shown in fig. 3.1, determine the transfer function  $G_{21}(s)$  and  $Z_{21}(s)$ . Also, find the driving point impedance  $Z_{11}(s)$ .


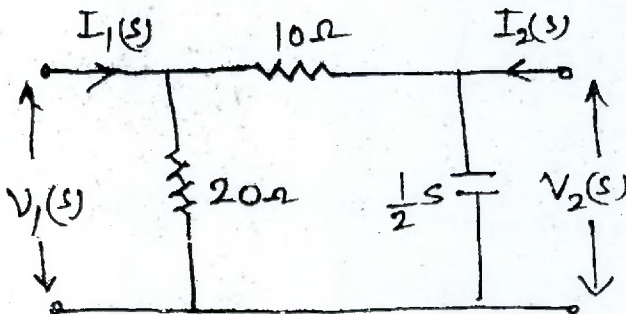


Figure 3.1

10

OR

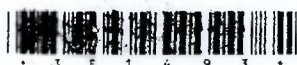

- 3 (a) For a given network function, draw the pole-zero diagram and hence deduce the time domain response  $i(t)$  :

$$I(s) = \frac{5s}{(s+1)(s^2+4s+8)}$$

8

- (b) How to determine the quality factors from the pole positions of a network function. For the given network function :

$$H(s) = \frac{10s}{s^2+30s+10^6}$$

Determine the resonant frequency lower and upper half-power frequencies, and quality factor.

8

### UNIT - IV

- 4 (a) Find the impedance parameters of following RC ladder network given in fig. 4.1.

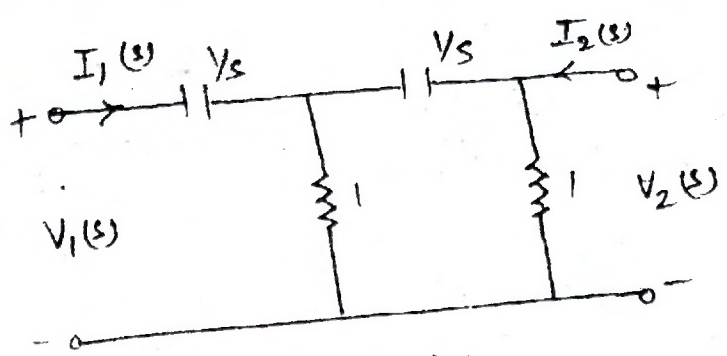


Figure 4.1

[Contd

(b) For the network shown in fig. 4.2, find Y-parameters.

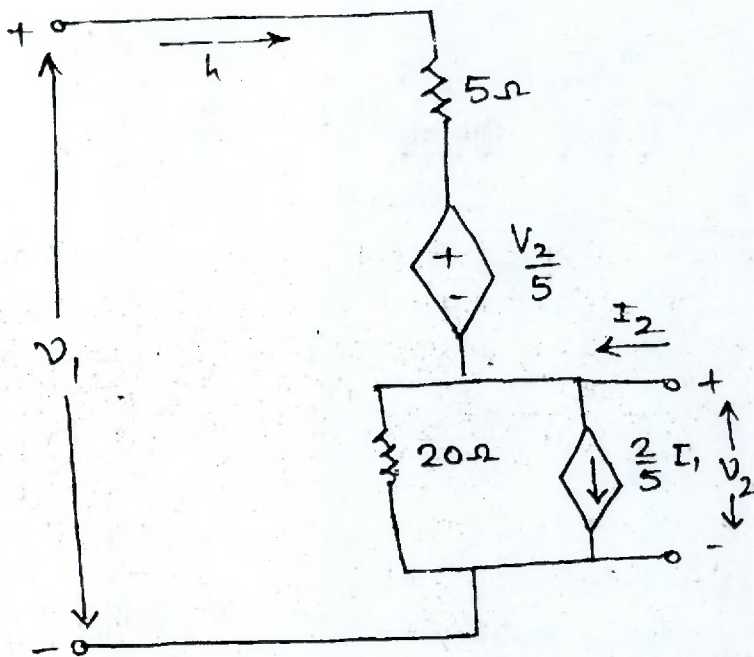


Figure 4.2

8

OR

4 (a) Determine  $Y_i$  for 3-terminal network given in fig. 4.3.

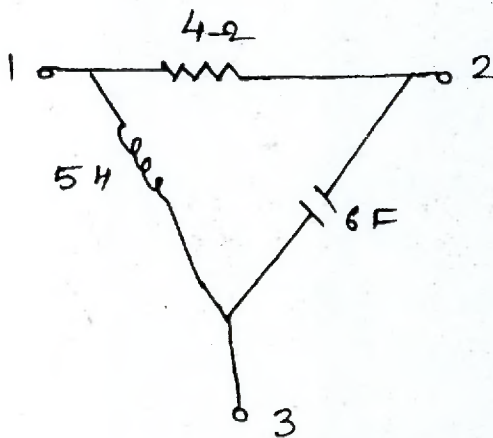


Figure 4.3

8



- (b) For the network given in fig. 4.4, determine the h-parameters at  $\omega = 10^8$  rad/sec.

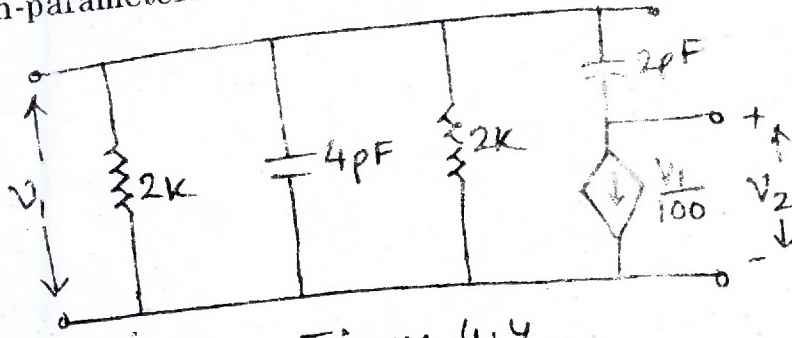


Figure 4.4

8

UNIT - V

- 5 (a) Show that the function  $\frac{s(3s+8)}{(s+1)(s+3)}$  represents an RL immittance. Also, realize the impedance in Foster form. 6
- (b) Find the Foster's I and II form and Cauer's I and II form of the RC driving point impedance :

$$Z_{RC}(s) = \frac{(s+2)(s+5)}{(s+1)(s+3)}$$

10

OR

- 5 (a) Check the following function for positive reality :

(i)  $Z(s) = \frac{(s^2 + 2s + 25)}{(s+4)}$

(ii)  $F(s) = \frac{(s^4 + 4s^3 + 5s^2 + 1)}{(s^4 + 2s^2 + 1)}$

3x2

- (b) An impedance function is given by :

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

Find the RC representation of :

- (i) Second Foster form  
 (ii) Second Cauer form.

10

