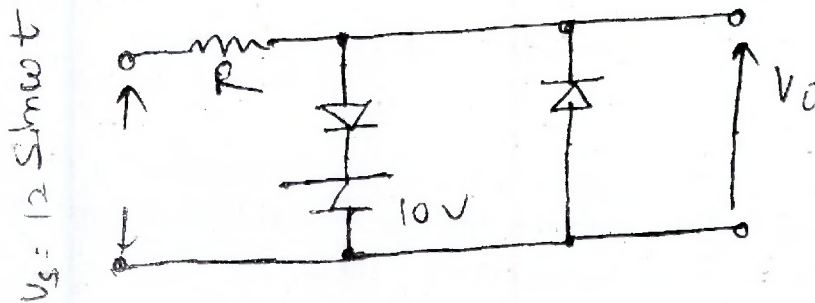


UNIT - II

- 2 (a) A diode whose internal resistance is 35Ω is to supply power to a $1k\Omega$ load from a $220V$ (rms) supply. Calculate :
- Peak load current
 - D.C. load current
 - A.C. load current
 - Diode voltage
 - Total input power to the circuit and
 - Percentage regulation from no load to given load.
- 10
- (b) Draw the characteristics of UJT and explain its working. 6

OR

- 2 (a) Draw the output waveform for the circuit given.



- (b) A full wave rectifier is to be designed to produce a peak output voltage $12V$ and delivers a current of 120 mA to the load. It is required to restrict the ripple of not more than 5% . An Input line voltage is $120V$ (rms), 60 Hz is available.
- 6
- 10

UNIT - III

- 3 (a) Write the Ebers and Moll equations. Sketch the circuit model, which satisfies these equations.
- 10

[Contd...]



(b) Define stabilization techniques and compensation techniques.

6

OR

3 (a) Discuss thermal runaway and define thermal resistance. What is the condition for thermal stability? - Explain.


8

(b) Explain base width modulation (the early effect) with the aid of plots of potential and minority concentration throughout the base region.

8

UNIT - IV

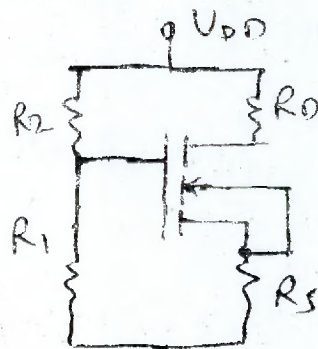4 (a) The n-channel enhancement mode MOSFET of figure is characterized by $V_T = 4V$ and $I_{Don} = 10 mA$. Assume negligible gate current, $R_1 = 50 K\Omega$, $R_2 = 0.4 M\Omega$, $R_s = 0$, $R_D = 2 K\Omega$ and $V_{DD} = 15V$. Find (i) V_{GSQ} (ii) I_{OQ} and (iii) V_{DSQ} .



8

(b) Define the working of FET as voltage variable resistor.

8

OR



- 4 (a) Sketch the circuit of CS amplifier. Derive the expression for the voltage gain at low frequencies. What is the maximum value of A_v ? 10
- (b) Draw the biasing circuit for a JFET or a depletion type MOSFET. Explain under what circumstances each of these two arrangements should be used. 6

UNIT - V

- 5 (a) Draw a Darlington emitter follower and explain, why the input impedance is higher than that of a single stage emitter follower. 10
- (b) State Miller's theorem with the aid of a circuit diagram. Repeat for the dual of Miller's theorem. 6

OR

- 5 (a) Derive the expression for the CE short circuit current gain A_i as a function of frequency. 8
- (b) Define f_β and f_T . What is the relationship between f_β and f_T ? 8

