

3E1401	Roll No. : _____	Total Printed Pages : 4
	3E1401	
<p>B. Tech. (Sem. III) (Reback) Examination, February - 2013 Applied Electronics & Inst. Engg. 3A12 Electronics Devices & Circuits (Common for BM, Ac, ME & PI)</p>		

Time : 3 Hours]

[Total Marks : 80

[Min. Passing Marks : 24

Attempt any five questions, selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of following supporting material is permitted during examination.

(Mentioned in form No. 205)

1. _____ Nil _____

2. _____ Nil _____

UNIT - I

1 (a) Describe the Hall effect ? What properties of a semiconductor are determined from a Hall effect experiment ?

8

(b) Define and explain the following terms :

(i) Mobility and conductivity

(ii) Fermi-Dirac distribution.

4+4=8

OR

1 (a) Explain Energy Band theory of crystals. On its basis bring out the difference between insulators, semiconductors and metals.

8



- (b) The resistivity of doped material is 0.039 ohm-cm . Calculate electron density and hole density, if $n_i = 2.5 \times 10^{13}/\text{cm}^3$, $\mu_e = 3600 \text{ cm}^2/\text{V-sec}$, $\mu_n = 1700 \text{ cm}^2/\text{V-sec}$.

8

UNIT - II


- 2 (a) Explain the load line concept as applicable to a diode circuit. How is the operating point shifted if the real is replaced by an ideal diode ?
- (b) What are voltage multiplier ? What is fundamental limitation of a voltage multiplier circuit compared to step up transformer ?

8

8

OR

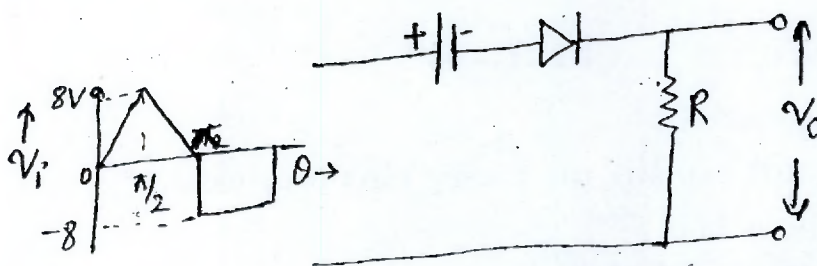- 2 (a) Find the output waveform for the circuit shown in Fig. (Assume ideal diode)



8

- (b) What do you understand by clamping circuit with neat diagram explain the action of :
- Positive clamping
 - Negative clamping.

8


UNIT - III

- 3 (a) Explain construction, characteristic and working principles of the following devices :
- LED
 - Photo diodes
 - Thermistors.

4×3=12

[Contd...]

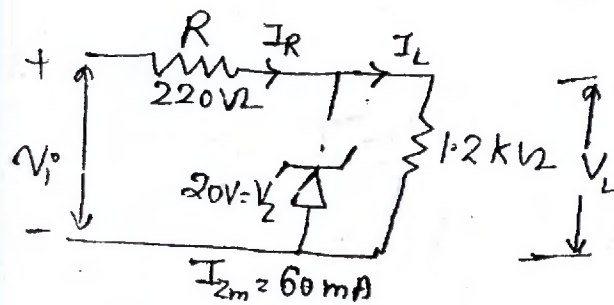- (b) Determine the range of values of V_i that will maintain the zener diode in ON state :



4

OR

- (a) Draw the load line for a solar cell. Find its maximum current and open circuit voltage across it. What is the maximum voltage we can get from a solar cell ?

8

- (b) Differentiate Zener and Avalanche breakdown. Also explain zener as a voltage regulator.

4

- (c) Why do we get negative resistance region in UJT characteristics ?

4

UNIT - IV

- (a) Draw and explain the biasing circuit in case of :

- Fixed bias
- Collector to base bias.

Derive expression for stability factor S in terms of circuit components for the above circuits.

8


- (b) Explain the early - effect in BJT. How it affects the output characteristics of a CE amplifier.

4


- (c) Explain "Thermal Runaway in BJT" and how it can be avoided.

4

OR

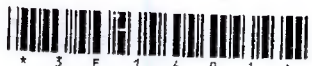

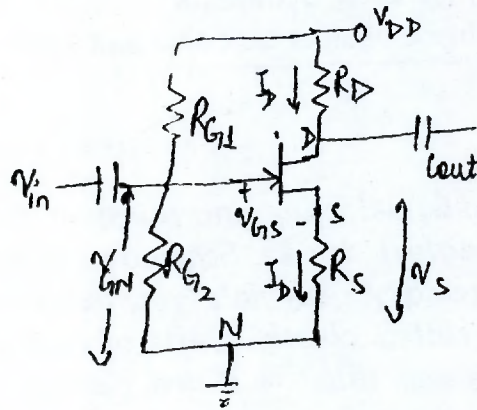- 4 (a) In a N-channel JFET determine the value of R_S to give operating point $I_D = 4 \text{ MA}$ and $V_{DS} = 8\text{V}$. Given that $V_{DD} = 25 \text{ V}$, $R_{G1} = 1.2 \text{ M}\Omega$, $R_{G2} = 0.6 \text{ M}\Omega$. JFET parameters are $V_P = -4\text{V}$ and $I_{DSS} = 12 \text{ MA}$.



- (b) Explain the working of FET as a voltage variable resistor. 8
- (c) Draw the circuit of JFET-CS amplifier using fixed bias and describe the working of biasing circuit. 4

UNIT - V

- 5 (a) Draw the small signal model of FET at low frequencies. In this model which parameters have been taken as independent and why? 6
- (b) State Miller's theorem and its dual with the help of a circuit diagram. 5
- (c) Explain the need and working principle of bootstrapping. 5

OR

- 5 (a) Write short notes on any two of the following : 4+4=8
- (i) Cascade amplifier
 - (ii) Differential amplifier
 - (iii) Darlington pair.
- (b) Draw and explain the working of two stage RC coupled amplifier circuit. 8