

OR

1. a) Find the pole - zero plots of the driving point and transfer impedance of the network given in fig.3 (8)

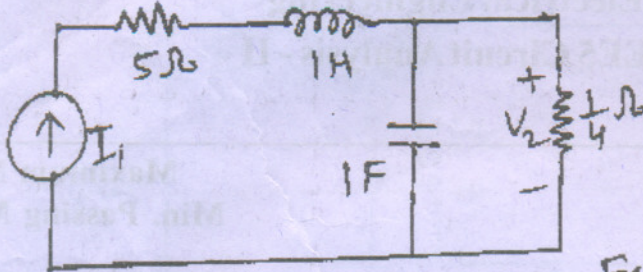


Fig 3

- b) A current transfer function is given by $I_s = \frac{5s}{(s+2)(s^2+2s+2)}$ obtain its time domain response. (8)

Unit - II

2. a) Test whether the following functions are Hurwitz or not. (8)

i) $s^5 + 3s^4 + 3s^3 + 4s^2 + s + 1$

ii) $s^4 + 3s^2 + 2$

- b) Check whether the function $Z(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$ is a PR function. (8)

OR

2. a) The driving point impedance of a one port reactive network is given by

$$Z(s) = 4 \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 16)}$$

obtain the Foster First form of LC network realisation. (8)

- b) The driving point impedance of a reactive network is given by $Z(s) = \frac{s^4 + 4s^2 + 3}{2s^3 + 3s}$

Find the second form of Cauer network. (8)

Unit - III

3. a) Determine the Z - parameters of the network given in fig.4 (8)

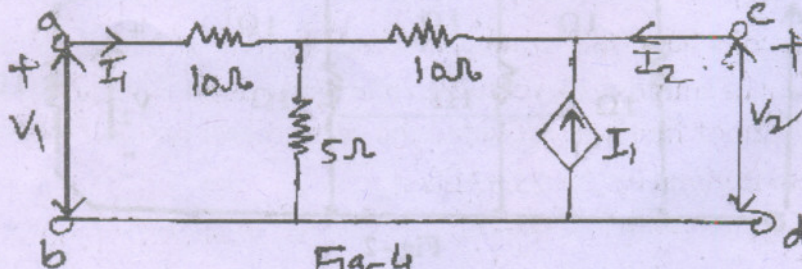


Fig-4