

- b) In the coupled coil circuit of fig.6, prove that $\frac{|I_1|}{|I_2|} = \frac{L_2}{M} \left[1 + \frac{R_2^2}{\omega^2 L_2^2} \right]^{1/2}$. (8)

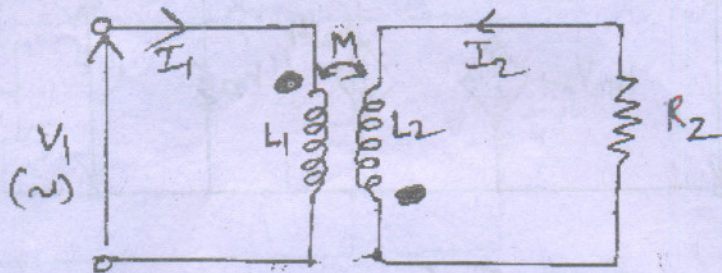


Fig. 6

OR

5. a) Two coupled coils have $K = 0.8$, $N_1 = 500$ turns, $N_2 = 1000$ turns and the mutual flux being 0.9 wb, find the primary coil flux. If the primary current be 10 A, find the primary coil inductance. Also obtain the secondary inductance. (8)
- b) Find V_2 in the circuit of fig.7 such that the current in the left hand loop (loop - 1) is zero. Assume $V_1 = 5 \angle 0^\circ$ V

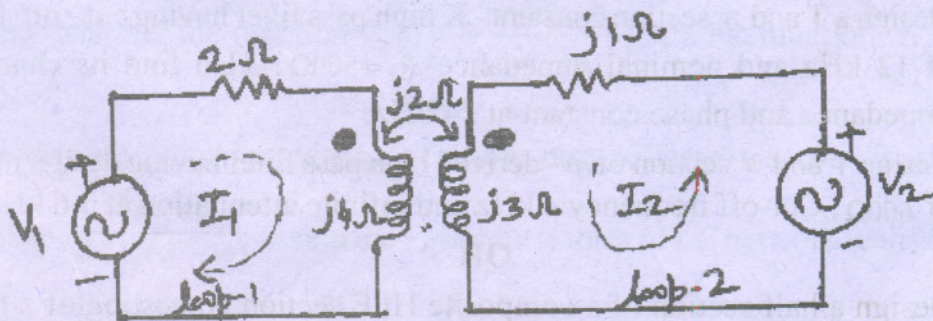


Fig-7