

Unit - II

2. a) Sketch a schmitt trigger circuit and explain its working principle. (8)
b) Explain how amplitude and frequency stability are improved in an oscillator. (8)
- Or
2. a) Explain Bar Khausen criteria in brief. (6)
b) Find the operating frequency of a ~~Hartley~~ Hartley oscillator if $L_1 = 100\mu\text{H}$ and $L_2 = 1\text{mH}$; Mutual inductance between coils $\mu = 20\mu\text{H}$ and $C = 20\text{PF}$. (10)

Unit - III

3. a) Explain and Draw the differential Amplifier with Darling ton connection, and also explain the DC Analysis. (8)
b) Give ideal versus Achial characteristics of OP-AMP. (8)
- Or
3. a) The input signal V_i to an Op-Amp is $0.03 \sin 1.5 \times 10^5 t$. What can be the maximum gain of an op-amp with flow rate of $0.4 \text{ v}/\mu\text{sec}$. (8)
b) Explain in brief five application of Op- Amp? (8)

Unit - IV

4. a) A ten bit D-A converter has a step size of 10mA . Find its maximum full scale output current and percent resolution. (8)
b) Explain series and shunt voltage regulators in brief. (8)

OR

4. a) Draw and explain internal structure of IC-555 timer? (8)
b) Explain performance measures of Regulated Power supply. Also give basic Aspects of Power Supply Characteristics. (8)

Unit - V

5. a) A class B transformer coupled Amplifier is to supply 4W to a 10Ω load. Available supply voltage $V_{cc} = 30\text{V}$. The transformer coefficient is 75% . Specify the output transistor and output transformer. (10)
b) Explain non linear distinction in Power Amplifier. (6)

OR

5. Write short notes on (any two) (8+8)
a) Quari-complementary symmetry amplifier.
b) Transformer coupled Audio Power Amplifier.
c) Higher order harmonic generation in Power Amplifier.