



Total Printed Pages : 4

3E-1462

Roll No. : _____

1462

B. E. - II Year (Sem. III) Examination, December - 2007

Electronic Device & Circuits

(Common to Computer Engg. & IT)

Time : 3 Hours]

[Total Marks : 80

[Min. Passing Marks : 24

Attempt overall 5 questions selecting one question from each unit.

All questions carry equal marks.

Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)

1. _____ Nil

2. _____ Nil

- 1 (a) Consider a circuit consisting of a diode D, a resistance R, and a signal source v_i in series.

Define :

- (1) Static characteristics
- (2) Dynamic characteristics
- (3) Transfer characteristics
- (4) Correlation between (ii) and (iii)

12

- (b) What is a comparator circuit ? How does such a circuit differ from a clipping circuit ?

4

OR

- 1 (a) Sketch the circuit for full wave rectifier. Derive the expressions for
- (1) dc current
 - (2) dc load voltage
 - (3) dc diode voltage
 - (4) the rms current


12

3E-1462]

1

[Contd...

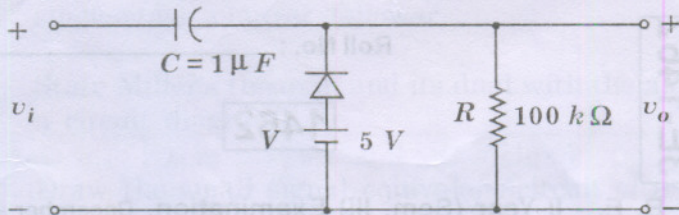- (b) Explain the circuit given below with the help of suitable input



- 2 Explain the construction and working principle of following devices :

- (1) VJI
- (2) Phototransistor
- (3) LDR
- (4) Solar cell.

16

OR

- 2 (a) For a phototransistor in the active region, write the expression for the collector current. Define all terms. Sketch the family of output characteristics.

8

- (b) Derive the equation for the volt-ampere characteristics of a photodiode. Define each symbol in the equation.

8

- 3 (a) For a p-n-p transistor biased in active region plot (in each region E, B and C) :

- (i) the potential variation
- (ii) the minority-carrier concentration
- (iii) indicate the various electron and hole current components crossing each junction.

8

- (b) Draw a family of CS drain characteristics of an n-channel JFET. Explain the shape of these curves qualitatively. Define the pinch-off voltage V_p .

8

OR

- 3 (a) Explain the h-parameter model of a transistor at low frequencies and derive the formulas for :
- (1) Current gain
 - (2) Voltage gain
 - (3) Input impedance.

12

- (b) Draw a self-bias circuit. Explain why such a circuit is an improvement over fixed-bias circuit.

4


- 4 Shown in figure below is a two-stage amplifier circuit in a CE-CC configuration. The transistor parameters are

$$h_{ie} = 2\text{ k}, h_{fe} = 50, h_{re} = 6 \times 10^{-4}$$

$$h_{ic} = 2\text{ k}, h_{fc} = -51, h_{re} = 1$$

$$h_{oe} = 25\text{ }\mu\text{A/V}, h_{oc} = 25\text{ }\mu\text{A/V}$$

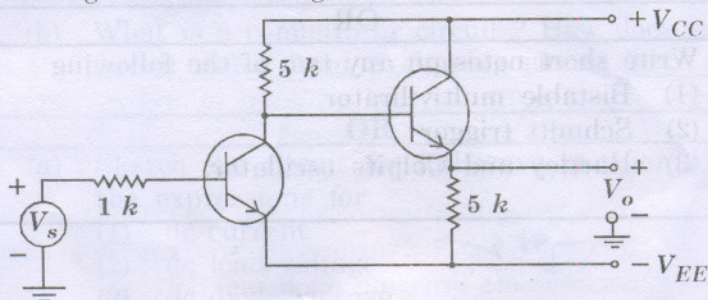Find the input and output impedances and overall voltage and current gains



16

OR

4	(a) Draw a Darlington emitter follower. Explain why the input impedance is higher than that of a single-stage emitter follower.	4
	(b) State Miller's theorem and its dual with the aid of a circuit diagram.	4
	(c) Draw the small signal equivalent circuit of a CS (common-source) amplifier and derive the expression for voltage gain.	8

5	(a) What are the four possible topologies of a feedback amplifier ? Identify the output signal X_o and the feed back signal X_f for each topology.	4
	(b) Give the two Barkhausen conditions required in order for sinusoidal oscillator to be sustained. State the frequency stability criterion.	4
	(c) Draw and explain the circuit of a Wien bridge oscillator. What determines the frequency of oscillations ? Will oscillations take place if the bridge is balanced ? Explain.	8

OR

5	Write short notes on any two of the following :	
	(1) Bistable multivibrator	
	(2) Schmitt trigger	
	(3) Hartley and Colpits oscillator.	8+8